

Exercises and Complements for the Introduction to Physics II

for Students

of Biology, Pharmacy and Geoscience

Sheet 6 / 08.04.2021


Zoom - Q&A on the Exercises: **20.04.2021-22.04.2021**

Exercise 21.

In an AC circuit ($U_{eff} = 220 \text{ V}$, $I_{eff} = 100 \text{ A}$, $f = 50 \text{ Hz}$), a coil and an ohmic resistor are connected in series. The time averaged value of the electrical power is $\overline{P} = 15 \text{ kW}$.

- (a) Calculate the power factor $\cos(\varphi)$ and the phase angle φ between current and voltage.
- (b) What additional capacitance had to be connected in series to the circuit to bring the power factor to $\cos(\varphi') = 0.9$?

Exercise 22.

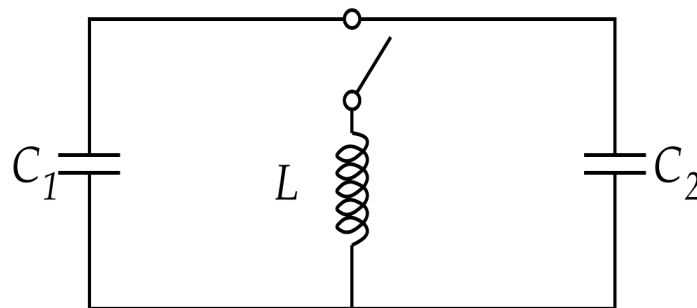

A resonant circuit consists of an ideal coil $L = 2,5 \text{ mH}$ and the capacitors $C_1 = 2 \mu\text{F}$ and $C_2 = 3 \mu\text{F}$. The capacitors were charged with $U = 180 \text{ V}$. Then, the switch is closed.

- a) How large is the oscillation period?
- b) Calculate the energies in the capacitors.
- c) Determine the maximum current amplitude at the coil.

Exercise 23.

A RLC -circuit is connected to a sine wave-generator with tunable frequency f and constant amplitude $U_m = 10$ V ($R = 1.0 \cdot 10^2 \Omega$, $C = 0.10 \mu\text{F}$, $L = 0.245$ H).

- (a) What does “resonance” mean? At what frequency f_0 will the resonance happen?
- (b) How large is the amplitude of the current I_m in the resonant case?
- (c) What is the voltage $U_{C,m}$ across the capacitor?

Exercise 24.

On the primary side of a voltage-reducing transformer 2.5 kV are fed, and loaded with 80 A on the secondary side. The ratio of the number of turns/windings on the primary and secondary sides is 20:1. Determine the voltage on the secondary side, the current on the primary side and the power output at an efficiency of 100% (ideal transformer)!

Answers.

Exercise 21. (a) 0.68 and 47.2° (b) 3.6 mF

Exercise 22. (a) $7.02 \cdot 10^{-4}$ s (b) $3.24 \cdot 10^{-2}$ J and $4.86 \cdot 10^{-2}$ J (c) 8.05 A

Exercise 23. (a) 1.02 kHz (b) 100 mA (c) 157 V

Exercise 24. 125 V, 4 A, 10 kW