

Departement Physik  
Universität Basel  
Prof. E. Meyer / PD. T. Glatzel  
Contact person: Miguel J. Carballido  
miguel.carballido@unibas.ch  
Office: 1.12  
Tel.: +41 (0)61 207 36 91  
<http://adam.unibas.ch>

---

---

Exercises and Complements for the Introduction to Physics II  
for Students  
of Biology, Pharmacy and Geoscience

---

---

Sheet 4 / 23.03.2022

Discussion: **29.03.2022 / 30.03.2022**

**Exercise 13.**

A current is transported via a high-voltage wire made of Copper (density  $\rho_M = 9.0 \cdot 10^3 \text{ kg}\cdot\text{m}^{-3}$ , atomic mass  $M_A = 63.3 \cdot 10^{-3} \text{ kg}\cdot\text{mol}^{-1}$ ) and of length 10 km (diameter  $d = 2 \text{ cm}$ ).

- (a) Determine the resistance of the wire ( $\rho_{Cu} = 1.7 \times 10^{-8} \text{ }\Omega\text{m}$ ).
- (b) A current  $I = 100 \text{ A}$  flows through the wire, and at the beginning of the line a voltage of 220 V is given. What is the voltage at the end of the wire, and therefore the voltage drop?
- (c) How long does an electron need on average to travel from the beginning to the end of the wire?

**Hint:** Assume that only one electron per Cu-atom contributes to the conductivity.


**Exercise 14.**

The salt content in human blood is 9 g per Liter. In order to investigate the electrical conductivity of blood, consider a saline solution containing 9 g NaCl dissolved in 1000 g  $\text{H}_2\text{O}$ .

- (a) What is the conductivity of this solution? The mobilities  $b$  of the ions are  $4.6 \cdot 10^{-8} \text{ m}^2/\text{Vs}$  (Na) and  $6.85 \cdot 10^{-8} \text{ m}^2/\text{Vs}$  (Cl).
- (b) Estimate the resistance of the human body between the two hands. The distance between hands is  $\approx 1.5 \text{ m}$ , and the cross-section of a hand is  $\approx 10 \text{ cm}^2$ .
- (c) If 100 mA current flows through the chest cavity, it is lethal. Which voltages are therefore dangerous?

**Exercise 15.**

Imagine a cube with twelve edges, consisting of twelve identical resistors  $R$  (see figure on the right). Determine the total resistance of the whole cube, if an electric voltage is applied between the points 1 and 7.

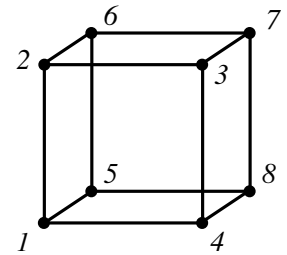

**Exercise 16.**

Consider the cube from exercise 15 and define an electrical network spanned by the path(s) between points i) 1 and 3, ii) 1 and 2. Determine the total resistance of both networks.

**Answers.**

Exercise 13. (a)  $0.54 \Omega$  (b) 54 V, respectively 166 V (c)  $4.3 \cdot 10^8$  s

Exercise 14. (a)  $1.7 \Omega^{-1} \text{m}^{-1}$  (b)  $882 \Omega$  (c) 88 V

Exercise 15.  $5R/6$

Exercise 16.  $7R/12$  und  $3R/4$