

Exercises and Complements for the Introduction to Physics II  
 for Students  
 of Biology, Pharmacy and Geoscience

Sheet 6 / 06.04.2022


Discussion: **12.04.2022 / 13.04.2022**

**Exercise 21.**

In an AC circuit ( $U_{eff} = 220 \text{ V}$ ,  $I_{eff} = 100 \text{ A}$ ,  $f = 50 \text{ Hz}$ ), a coil and an ohmic resistor are connected in series. The time averaged value of the electrical power is  $\overline{P} = 15 \text{ kW}$ .

- (a) Calculate the power factor  $\cos(\varphi)$  and the phase angle  $\varphi$  between current and voltage.
- (b) What additional capacitance had to be connected in series to the circuit to bring the power factor to  $\cos(\varphi') = 0.9$ ?

**Exercise 22.**

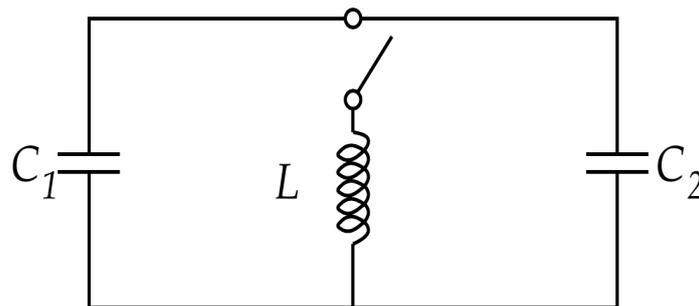

A resonant circuit consists of an ideal coil  $L = 2,5 \text{ mH}$  and the capacitors  $C_1 = 2 \mu\text{F}$  and  $C_2 = 3 \mu\text{F}$ . The capacitors were charged with  $U = 180 \text{ V}$ . Then, the switch is closed.

- a) How large is the oscillation period?
- b) Calculate the energies in the capacitors.
- c) Determine the maximum current amplitude at the coil.

**Exercise 23.**

A  $RLC$ -circuit is connected to a sine wave-generator with tunable frequency  $f$  and constant amplitude  $U_m = 10$  V ( $R = 1.0 \cdot 10^2 \Omega$ ,  $C = 0.10 \mu\text{F}$ ,  $L = 0.245$  H).

- (a) What does “resonance” mean? At what frequency  $f_0$  will the resonance happen?
- (b) How large is the amplitude of the current  $I_m$  in the resonant case?
- (c) What is the voltage  $U_{C,m}$  across the capacitor?

**Exercise 24.**

On the primary side of a voltage-reducing transformer 2.5 kV are fed, and loaded with 80 A on the secondary side. The ratio of the number of turns/windings on the primary and secondary sides is 20:1. Determine the voltage on the secondary side, the current on the primary side and the power output at an efficiency of 100% (ideal transformer)!

**Answers.**

Exercise 21. (a) 0.68 and  $47.2^\circ$  (b) 3.6 mF

Exercise 22. (a)  $7.02 \cdot 10^{-4}$  s (b)  $3.24 \cdot 10^{-2}$  J and  $4.86 \cdot 10^{-2}$  J (c) 8.05 A

Exercise 23. (a) 1.02 kHz (b) 100 mA (c) 157 V

Exercise 24. 125 V, 4 A, 10 kW